

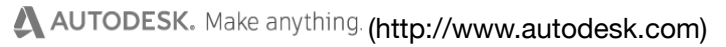


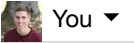



Download  
Let's Make ...

 

Technology (/technology/) &gt; Arduino | by AaronB299 (/member/AaronB299/) Follow

Posted Feb. 12, 2018 | Stats |  CC BY-NC-SA[editInstructable/edit/E54VTICJDKKDQLD/](#)

## Step 1: Add Basic Components

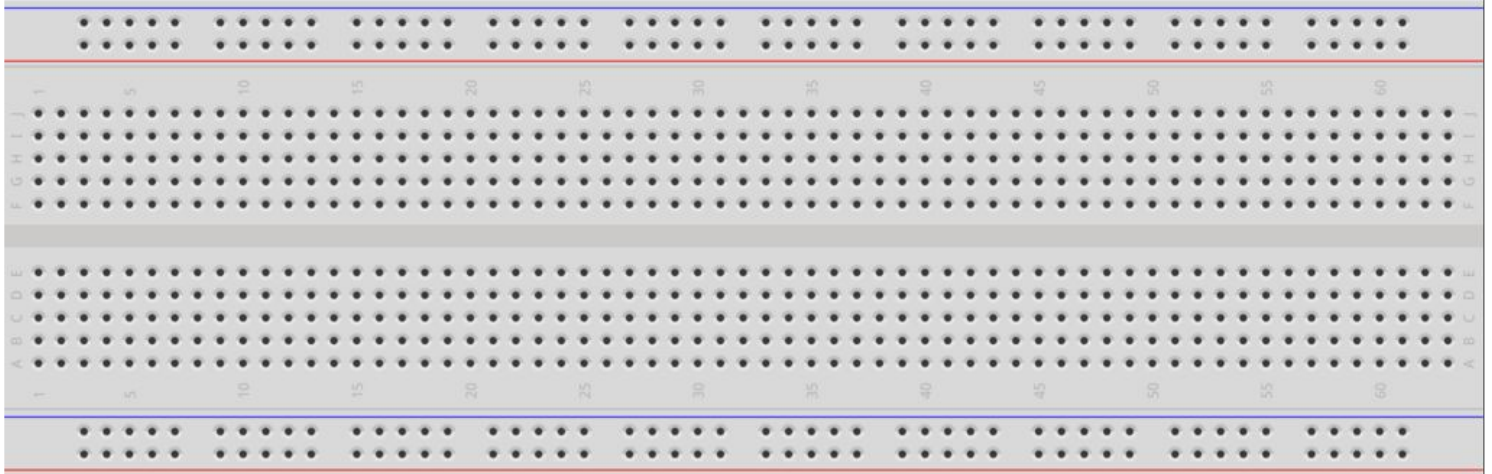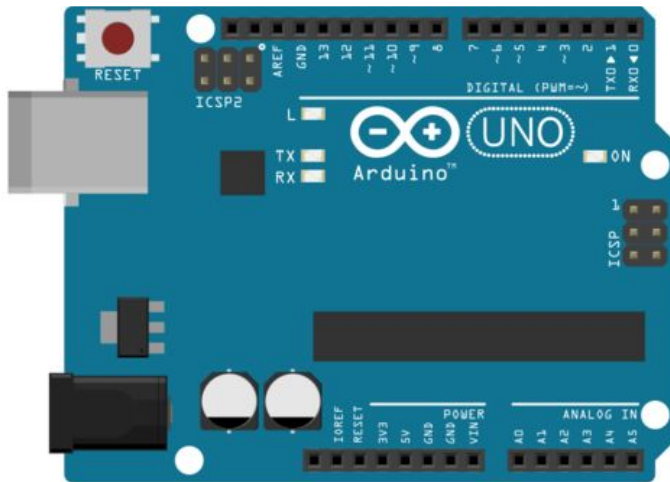

(<https://cdn.instructables.com/EIV/1EAV/IDKKDPMF/EIV/1EAV/IDKKDPMF/LARGE.png>)

fritzing

1. Add Arduino UNO R3
2. Add a full sized breadboard

Add Tip


Ask Question
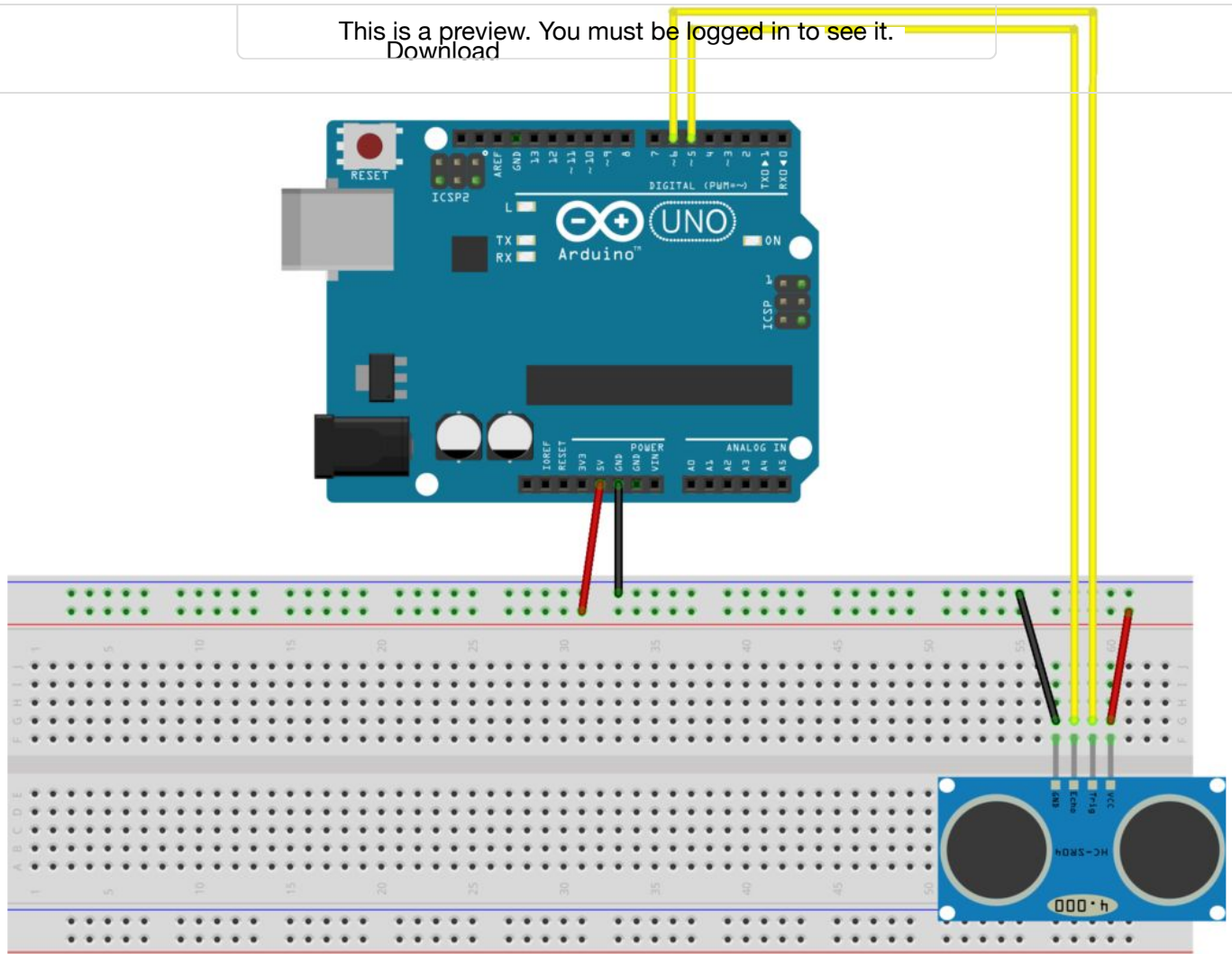
## Step 2: Add Ultrasonic Sensor

Author

[editInstructable/edit/E54VTICJDKKDQLD/](#)





<https://cdn.instructables.com/ECS/5VEY/IDKKDPKO/ECS5VEYIDKKDPKO.LARGE.jpg> fritzing


1. Add ultrasonic HC-SR04 sensor
2. Connect 5V to power rail of breadboard
3. Connect GRN (ground) to the grounded rail of the breadboard
4. Connect GRN on the ultrasonic sensor to the grounded rail of the breadboard
5. Connect Echo on the ultrasonic sensor to pin 5 on the Arduino UNO
6. Connect Trig on the ultrasonic sensor to pin 6 on the Arduino UNO
7. Connect Vcc on the ultrasonic sensor to the power rail of the breadboard

Add Tip

Ask Question **Author**

[editInstructable/edit/E54VTICJDKKDQLD/](https://www.instructables.com/edit/E54VTICJDKKDQLD/)

## Step 3: Add LCD Screen

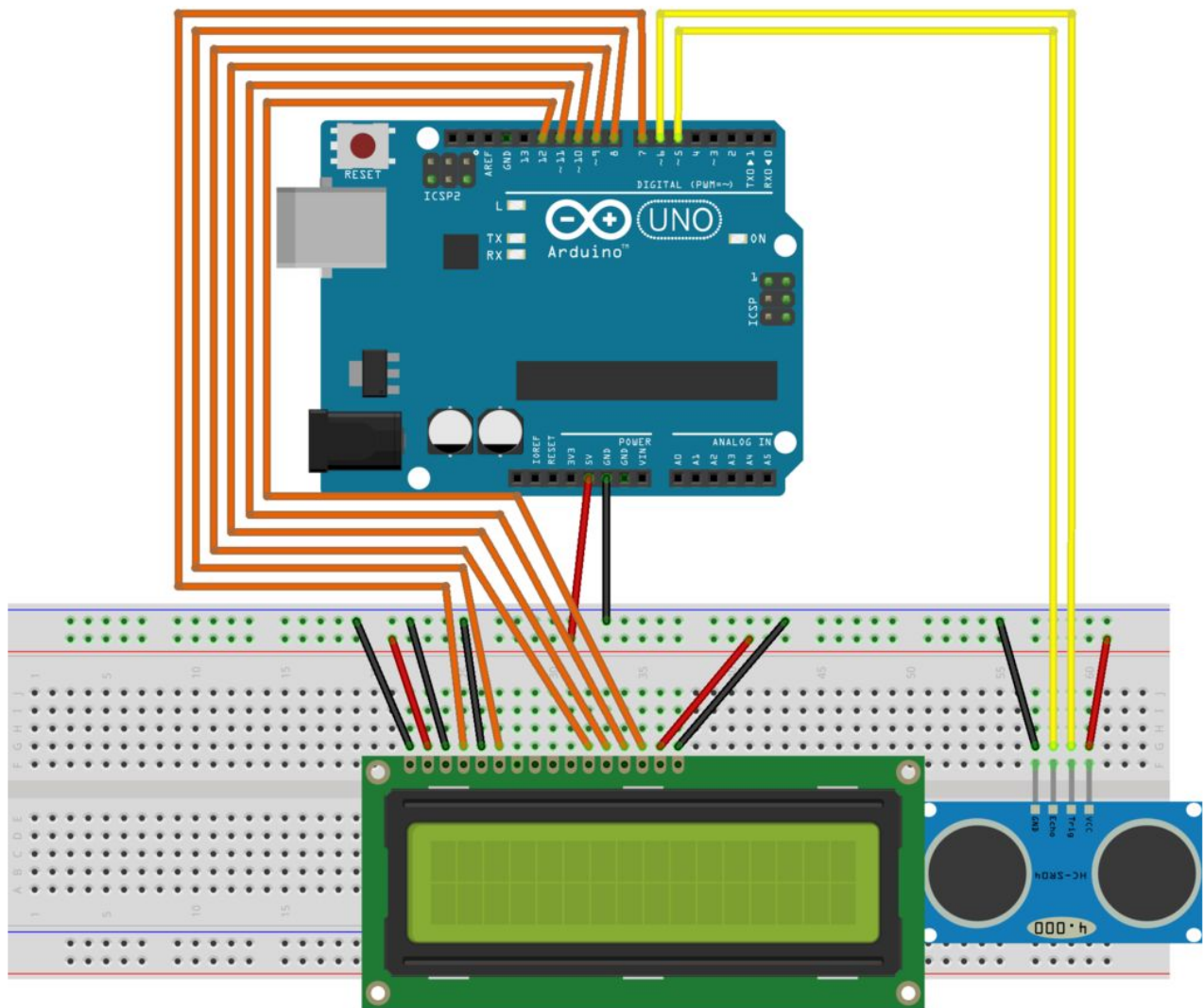

<https://cdn.instructables.com/E7KAC1Q/IDKKDLYS/E7KAC1Q-IDKKDLYS-LARGE.jpg> fritzing

The LCD screen's pins must be connected to the breadboard and Arduino UNO R3 in the following order. From left to right with the left starting at pin 1 and ending at the right with pin 16:

1. Ground
2. Power
3. Ground
4. Pin 7

**Author**

[editInstructable/edit/E54VTICJDKKDQLD/](https://www.instructables.com/edit/E54VTICJDKKDQLD/)

5. Ground

This is a preview. You must be logged in to see it.  
Download

6. Pin 8

7. Leave empty

8. Leave empty

9. Leave empty

10. Leave empty

11. Pin 9

12. Pin 10

13. Pin 11

14. Pin 12

15. Power

16. Ground

Add Tip

Ask Question

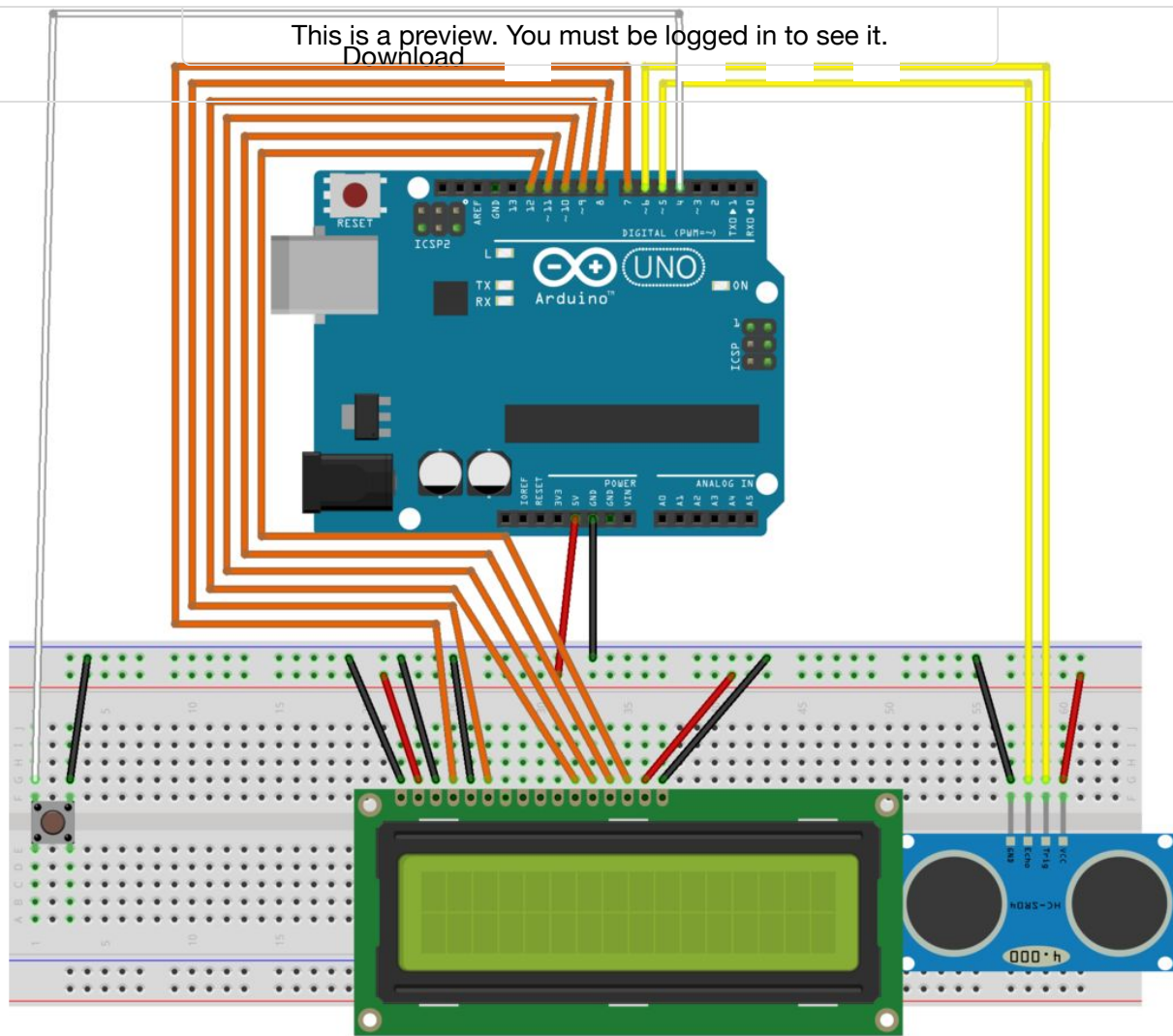
## Step 4: Add a Push Button

Author



[editInstructable/edit/E54VTICJDKKDQLD/](#)





<https://cdn.instructables.com/EPB/4WVQ/IDKKDQWYB/EPB4WVQIDKKDQWYB/LARGE.jpg> fritzing

1. Add a push button
2. Connect the upper right corner to the ground breadboard rail
3. Connect the upper left corner to pin 4

**Note:** for all buttons, they will have a complete circuit until the button is pressed closing the circuit. This is required because we will add a total of 4 buttons and only 4 digital pins remaining, one of which is digital pin 13. Pin 13 is harder to use as an input because it has an LED and resistor attached. Thus, this weird trick is warranted.

Add Tip


Ask Question

Author

[editInstructable/edit/E54VTICJDKKDQLD/](https://www.instructables.com/edit/E54VTICJDKKDQLD/)



## Step 5: Add the Other 3 Buttons

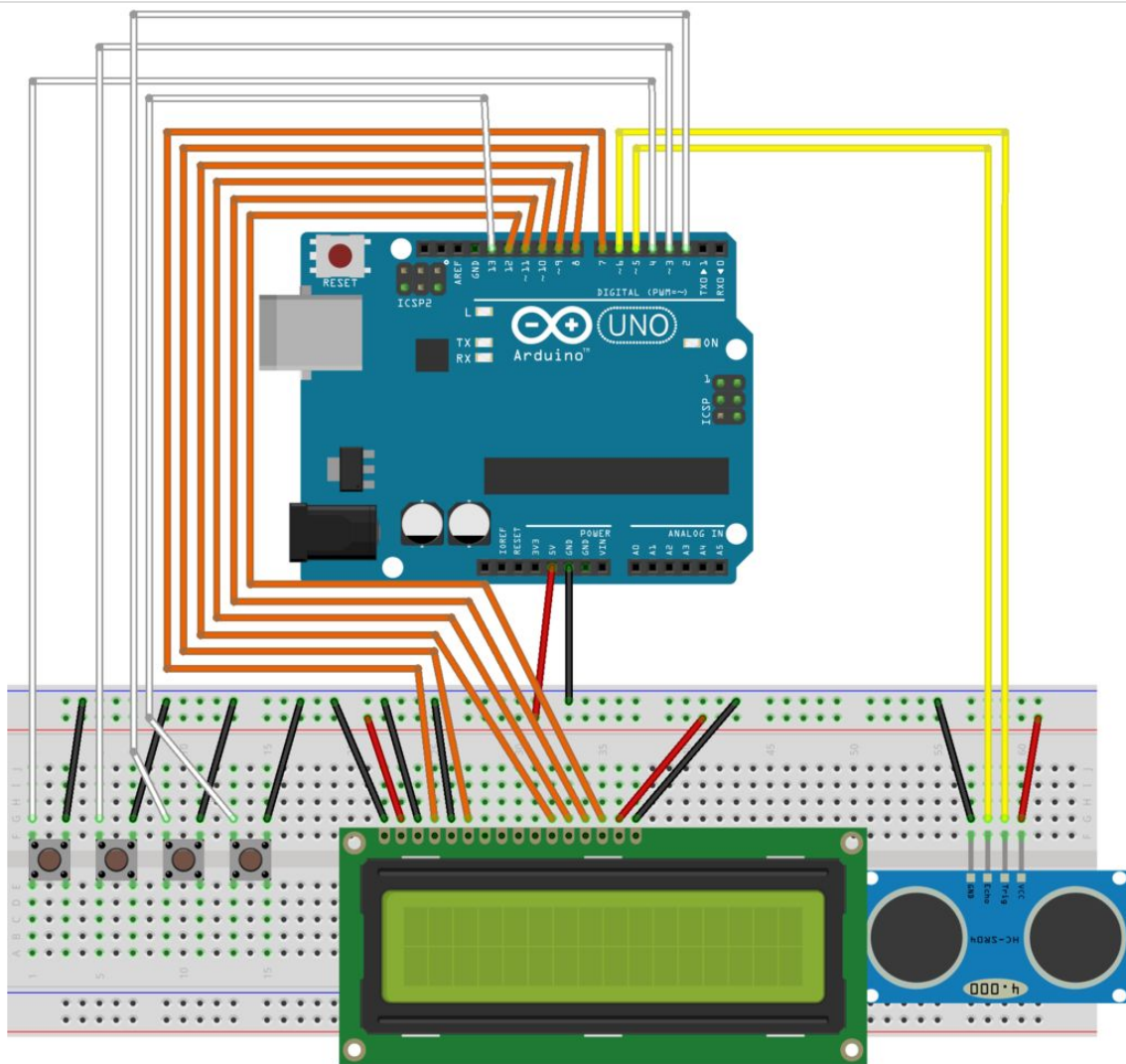

<https://cdn.instructables.com/E42/0B4D/IDKKDVS7/E420B4DIDKKDVS7/LABCE.jpg>

Button number 1 is on the left, to the right of it is considered button 2, to the right of button 2 is button 3, and at the far end is button 4. Adding the other 3 buttons is just like adding the first:

1. Add 3 push buttons
2. Ground the 3 push buttons
3. Connect button 2's output to pin 3
4. Connect button 3's output to pin 2
5. Connect button 4's output to pin 13

**Author**

[editInstructable/edit/E54VTICJDKKDQLD/](https://www.instructables.com/edit/E54VTICJDKKDQLD/)

Note: Check the completed diagram carefully. You need to be logged in to see it.

Add Tip

Ask Question

## Step 6: Add Code

1. Download the code
2. Open up the code
3. Connect Arduino UNO R3 to the computer
4. Upload the code to the Arduino UNO

aaron barlow ultrasonic

Download (<https://cdn.instructables.com/ORIG/FVC/9ET0/JDKKDZPL/FVC9ET0JDKKDZPL.ino>)

(<https://cdn.instructables.com/ORIG/FVC/9ET0/JDKKDZPL/FVC9ET0JDKKDZPL.ino>)

Add Tip

Ask Question

## Step 7: Done

What did you design? An ultrasonic alarm system that has 3 levels of safety detection! The LCD and serial output monitor allow one to observe the 3 levels of safety as well as other useful information. You can also disarm the alarm at anytime by pressing button 1, 2, and 4 in that order and only that order. The alarm will be re-armed within 5 seconds or when the passcode is successfully re-entered.

Author

[editInstructable/edit/E54VTICJDKKDQLD/](https://www.instructables.com/edit/E54VTICJDKKDQLD/)





When one gets within 25 centimeters, the alarm will ring for 10 seconds and will remain locked for 10 seconds unless the alarm is disarmed. Within 60 centimeters, the alarm will tell you it is the final warning. Otherwise, outside that distance, the alarm informs you to stay back with a safety level of 1.

You can also download the Fritzing Diagram if desired.

**sonic.fzz**

Download (<https://cdn.instructables.com/ORIG/FGO/979U/JDKKE21W/FGO979UJDKKE21W.fzz>)  
(<https://cdn.instructables.com/ORIG/FGO/979U/JDKKE21W/FGO979UJDKKE21W.fzz>)

Add Tip

Ask Question

## Share

Did you make this project?

Share it with us!

I Made It!

## Recommendations



Add Tip

**Author**

[editInstructable/edit/E54VTICJDKKDQLD/](#)





This is a preview. You must be logged in to see it.

Download

Ask Question




Post Comment

We have a be nice policy.  
Please be positive and constructive.

Add Images

Post

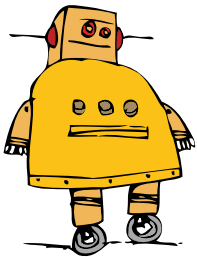

## Newsletter

Let your inbox help you discover our best projects, classes, and contests. Instructables will help you learn how to make anything!

enter email

I'm in!

## About Us

[Who We Are \(/about/\)](/about/)

[Advertise \(/advertise/\)](/advertise/)

[Contact \(/about/contact.jsp\)](/about/contact.jsp)

[Jobs \(/community/Positions-available-at-Instructables/\)](/community/Positions-available-at-Instructables/)

[Help \(/id/how-to-write-a-great-instructable/\)](/id/how-to-write-a-great-instructable/)

Author



[editInstructable/edit/E54VTICJDKKDQLD/](#)